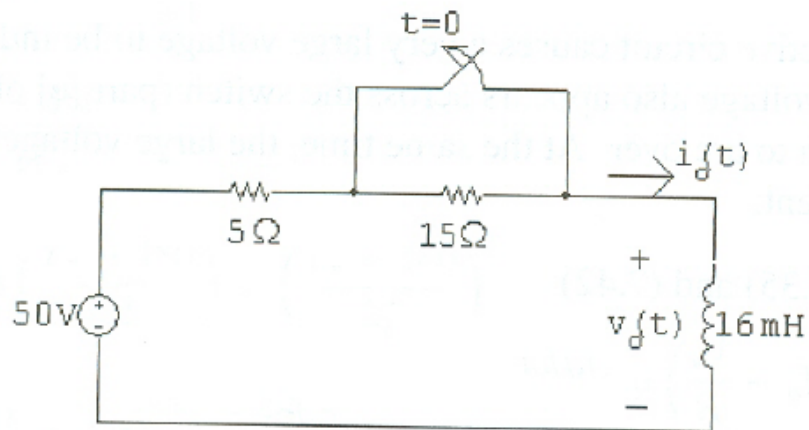


HW#11 Solutions

P 7.35 After making a Thévenin equivalent we have



For $t < 0$, the $15\ \Omega$ resistor is bypassed:

$$i_o(0^-) = i_o(0^+) = 50/5 = 10\ \text{A}$$

$$\tau = \frac{L}{R} = \frac{16 \times 10^{-3}}{5 + 15} = 8 \times 10^{-4}; \quad \frac{1}{\tau} = 1250$$

$$i_o(\infty) = \frac{V}{R_{\text{eq}}} = \frac{50}{5 + 15} = 2.5\ \text{A}$$

$$i_o = i_o(\infty) + [i_o(0^+) - i_o(\infty)]e^{-t/\tau} = 2.5 + (10 - 2.5)e^{-1250t} = 2.5 + 7.5e^{-1250t}\ \text{A}, t \geq 0$$

$$v_o = L \frac{di_o}{dt} = 16 \times 10^{-3}(-1250)(7.5e^{-1250t}) = -150e^{-1250t}\ \text{V}, \quad t \geq 0^+$$

P 7.36 [a] $v_o(0^+) = -I_g R_2; \quad \tau = \frac{L}{R_1 + R_2}$

$$v_o(\infty) = 0$$

$$v_o(t) = -I_g R_2 e^{-[(R_1 + R_2)/L]t} \text{ V}, \quad t \geq 0^+$$

[b] $v_o = -(10)(15)e^{-\frac{(5+15)}{0.016}t} = -150e^{-1250t} \text{ V}, \quad t \geq 0^+$

[c] $v_o(0^+) \rightarrow \infty$, and the duration of $v_o(t) \rightarrow$ zero

[d] $v_{sw} = R_2 i_o; \quad \tau = \frac{L}{R_1 + R_2}$

$$i_o(0^+) = I_g; \quad i_o(\infty) = I_g \frac{R_1}{R_1 + R_2}$$


Therefore $i_o(t) = \frac{I_g R_1}{R_1 + R_2} + \left[I_g - \frac{I_g R_1}{R_1 + R_2} \right] e^{-[(R_1 + R_2)/L]t}$

$$i_o(t) = \frac{R_1 I_g}{(R_1 + R_2)} + \frac{R_2 I_g}{(R_1 + R_2)} e^{-[(R_1 + R_2)/L]t}$$

Therefore $v_{sw} = \frac{R_1 I_g}{(1 + R_1/R_2)} + \frac{R_2 I_g}{(1 + R_1/R_2)} e^{-[(R_1 + R_2)/L]t}, \quad t \geq 0^+$

[e] $|v_{sw}(0^+)| \rightarrow \infty; \quad \text{duration} \rightarrow 0$

P 7.47 For $t < 0$

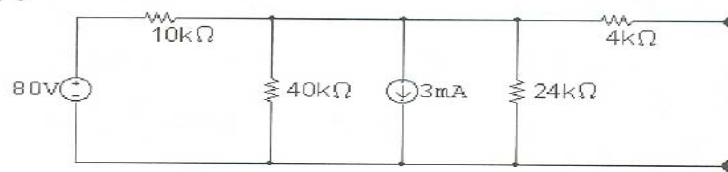


Simplify the circuit:

$$80/10,000 = 8 \text{ mA}, \quad 10 \text{ k}\Omega \parallel 40 \text{ k}\Omega \parallel 24 \text{ k}\Omega = 6 \text{ k}\Omega$$

$$8 \text{ mA} - 3 \text{ mA} = 5 \text{ mA}$$


$$5 \text{ mA} \times 6 \text{ k}\Omega = 30 \text{ V}$$

Thus, for $t < 0$

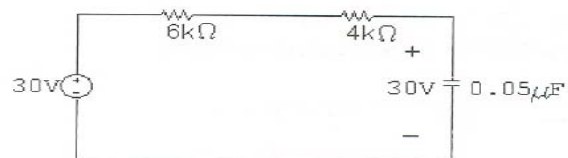

$$\therefore v_o(0^-) = v_o(0^+) = 30 \text{ V}$$

$t > 0$

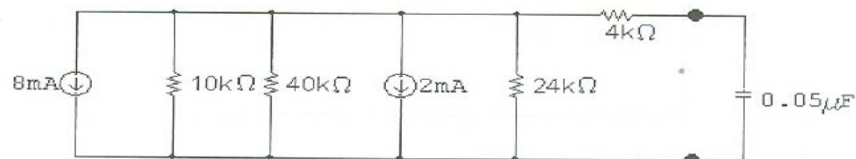


Simplify the circuit:

$$8 \text{ mA} + 2 \text{ mA} = 10 \text{ mA}$$

$$10 \text{ k}\Omega \parallel 40 \text{ k}\Omega \parallel 24 \text{ k}\Omega = 6 \text{ k}\Omega$$

$$(10 \text{ mA})(6 \text{ k}\Omega) = 60 \text{ V}$$

Thus, for $t > 0$

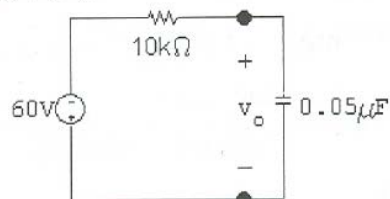


$$v_o(\infty) = -60 \text{ V}$$

$$\tau = RC = (10 \text{ k})(0.05 \mu) = 0.5 \text{ ms}; \quad \frac{1}{\tau} = 2000$$

$$v_o = v_o(\infty) + [v_o(0^+) - v_o(\infty)]e^{-t/\tau} = -60 + [30 - (-60)]e^{-2000t}$$

$$= -60 + 90e^{-2000t} \text{ V} \quad t \geq 0$$

P 7.50 [a] For $t > 0$:

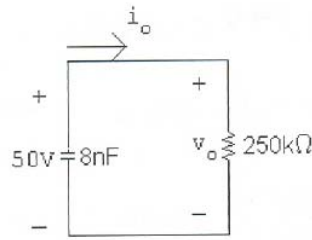


$$\tau = RC = 250 \times 10^3 \times 8 \times 10^{-9} = 2 \text{ ms}; \quad \frac{1}{\tau} = 500$$

$$v_o = 50e^{-500t} \text{ V}, \quad t \geq 0^+$$

$$\text{[b]} \quad i_o = \frac{v_o}{250,000} = \frac{50e^{-500t}}{250,000} = 200e^{-500t} \mu\text{A}$$

$$v_1 = \frac{-1}{40 \times 10^{-9}} \times 200 \times 10^{-6} \int_0^t e^{-500x} dx + 50 = 10e^{-500t} + 40 \text{ V}, \quad t \geq 0$$

P 7.53 [a]

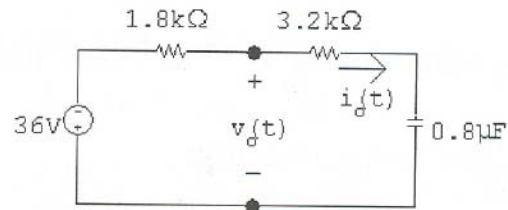

$$i_o(0^+) = \frac{-36}{5000} = -7.2 \text{ mA}$$

$$\text{[b]} \quad i_o(\infty) = 0$$

$$\text{[c]} \quad \tau = RC = (5000)(0.8 \times 10^{-6}) = 4 \text{ ms}$$

$$\text{[d]} \quad i_o = 0 + (-7.2)e^{-250t} = -7.2e^{-250t} \text{ mA}, \quad t \geq 0^+$$

$$\text{[e]} \quad v_o = -[36 + 1800(-7.2 \times 10^{-3}e^{-250t})] = -36 + 12.96e^{-250t} \text{ V}, \quad t \geq 0^+$$