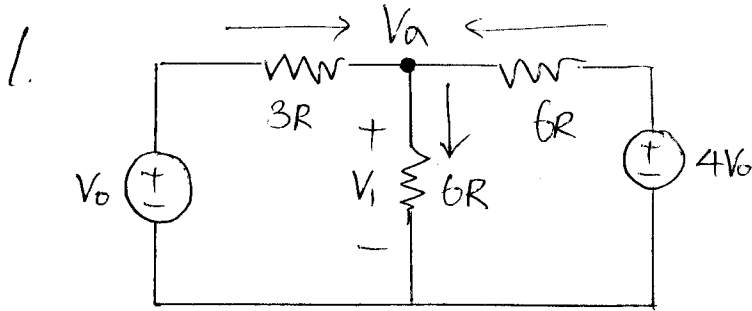


Homework #1 Solution



$$\frac{V_0 - V_a}{3R} + \frac{4V_0 - V_a}{6R} = \frac{V_a}{6R} \quad \text{--- (1)}$$

$$V_a = V_i \quad \text{--- (2)}$$

By (1) $\times 6R$,


$$2(V_0 - V_a) + 4V_0 - V_a = V_a \quad \text{--- (1')}$$

After regrouping terms,

$$4V_0 = 4V_a$$

$$V_a = 1.5V_0 = V_i \quad (\because (2))$$
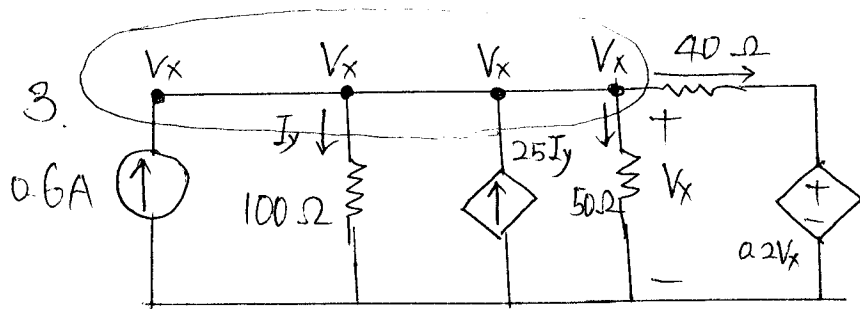
$$\therefore \underline{\underline{V_i = 1.5V_0}}$$



$$0.6 + 25I_y = \frac{V_x}{100} + \frac{V_x}{50} + \frac{V_x - 0.2V_x}{40} \quad \text{--- (1)}$$

$$\frac{V_x}{100} = I_y \quad \text{--- (2)}$$

By ① × 200,

$$120 + 5000I_y = 2V_x + 4V_x + 4V_x \quad \text{--- (1')}$$

After regrouping terms,

$$10V_x - 5000I_y = 120 \quad \text{--- (1'')}$$


$$I_y = \frac{V_x}{100} \quad \text{--- (2)}$$

By applying ② to ①''.

$$10V_x - 5000\left(\frac{V_x}{100}\right) = 120$$

$$V_x = -3(V)$$
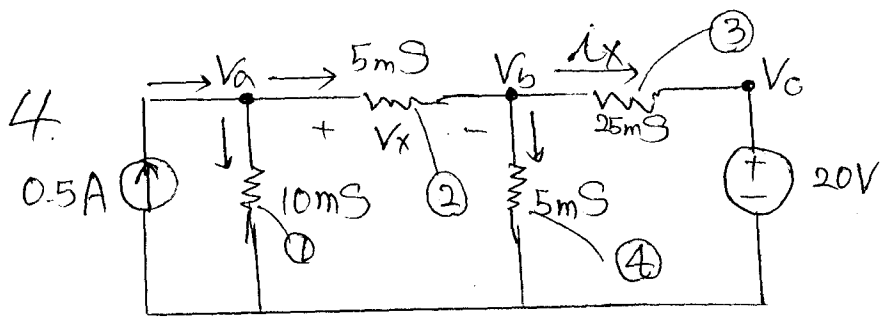
$$\therefore \underline{\underline{V_x = -3V}}$$



Reference node d.

(a) A voltage source ties node c to the reference node.
Hence the node voltage V_c is fixed at 20V.

By applying KCL to node a, b.

$$0.5 = 0.01 V_a + 0.005 (V_a - V_b) \quad \text{--- (1)}$$

$$0.005 (V_a - V_b) = 0.005 V_b + 0.025 (V_b - 20) \quad \text{--- (2)}$$

After regrouping terms,

$$3V_a - V_b = 100 \quad \text{--- (1')}$$

$$V_a - 7V_b = -100 \quad \text{--- (2')}$$

Therefore,

$$\begin{pmatrix} 3 & -1 \\ 1 & -7 \end{pmatrix} \begin{pmatrix} V_a \\ V_b \end{pmatrix} = \begin{pmatrix} 100 \\ -100 \end{pmatrix}$$

$$(b) \begin{pmatrix} 3 & -1 \\ 1 & -7 \end{pmatrix}^{-1} = \frac{1}{3 \times (-7) - (-0.1)} \begin{pmatrix} -7 & 1 \\ -1 & 3 \end{pmatrix} = -\frac{1}{20} \begin{pmatrix} -7 & 1 \\ -1 & 3 \end{pmatrix}$$

$$\begin{pmatrix} 3 & -1 \\ 1 & -7 \end{pmatrix}^{-1} \begin{pmatrix} 3 & -1 \\ 1 & -7 \end{pmatrix} \begin{pmatrix} V_a \\ V_b \end{pmatrix} = \begin{pmatrix} 3 & -1 \\ 1 & -7 \end{pmatrix}^{-1} \begin{pmatrix} 100 \\ -100 \end{pmatrix}$$

$$\begin{pmatrix} V_a \\ V_b \end{pmatrix} = -\frac{1}{20} \begin{pmatrix} -7 & 1 \\ -1 & 3 \end{pmatrix} \begin{pmatrix} 100 \\ -100 \end{pmatrix}$$

$$\therefore \underline{V_a = 40V, V_b = 20V} = -\frac{1}{20} \begin{pmatrix} -7 \times 100 + 1 \times (-100) \\ -1 \times 100 + 3 \times (-100) \end{pmatrix} = \begin{pmatrix} 40 \\ 20 \end{pmatrix} = \begin{pmatrix} V_a \\ V_b \end{pmatrix}$$

4. (Continued)

$$(c) V_x = V_a - V_b = 40 - 20 = 20(V) =$$

$$V_{a1} = V_d - V_a = 0 - 40 = -40(V) =$$

$$V_{b1} = V_d - V_b = 0 - 20 = -20(V) =$$

$$(d) i_x = (V_b - V_c) 0.025 = 0 =$$

Therefore, the power delivered by voltage source is zero.

On the other hand, the power delivered by current source is as follows.

$$P_{\text{①}} = I V_a = (-0.5) \times 40 = -20(W)$$

The power absorbed by each resistor is as follows.

$$P_{\text{②}} = G V_a^2 = 0.01 \times 40^2 = 16(W)$$


$$P_{\text{③}} = G V_x^2 = 0.005 \times 20^2 = 2(W)$$

$$P_{\text{④}} = G V_b^2 = 0.005 \times 20^2 = 2(W)$$

$$P_{\text{⑤}} = 0$$

Total power absorbed by each resistor is $16 + 2 + 2 = 20(W)$

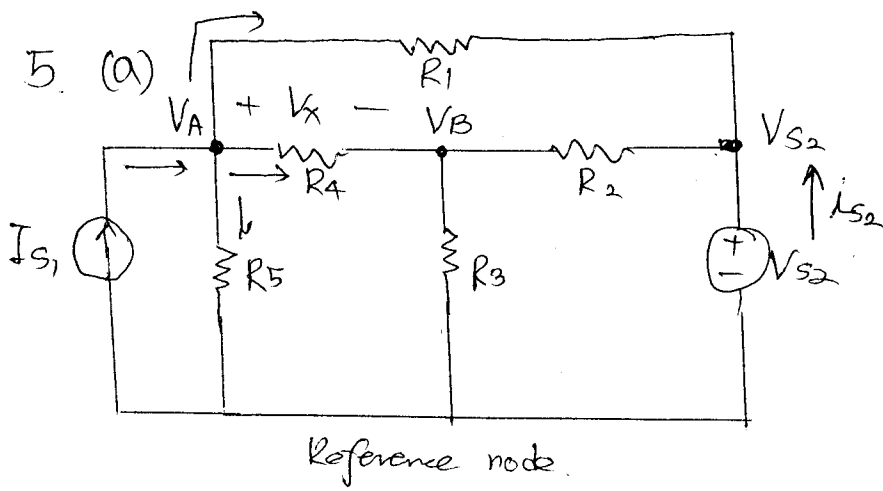Therefore, the principle of conservation of power is verified. \Rightarrow



$$I_{s1} = 4 \text{ mA}$$

$$V_{s2} = 20 \text{ V}$$

$$R_1 = 2.5 \text{ k}\Omega$$

$$R_2 = R_3 = R_4 = 10 \text{ k}\Omega, R_5 = 5 \text{ k}\Omega$$

By applying KCL to node A and B,

$$I_{s1} = \frac{V_A}{R_5} + \frac{V_A - V_B}{R_4} + \frac{V_A - V_{s2}}{R_1} \quad \text{--- (1)}$$

$$\frac{V_B - V_A}{R_4} + \frac{V_B}{R_3} + \frac{V_B - V_{s2}}{R_2} = 0 \quad \text{--- (2)}$$

After regrouping terms,

$$7V_A - V_B = 120 \quad \text{--- (1')}$$

$$-V_A + 3V_B = 20 \quad \text{--- (2')}$$

$$\begin{pmatrix} 7 & -1 \\ -1 & 3 \end{pmatrix} \begin{pmatrix} V_A \\ V_B \end{pmatrix} = \begin{pmatrix} 120 \\ 20 \end{pmatrix} \Rightarrow \begin{pmatrix} V_A \\ V_B \end{pmatrix} = \begin{pmatrix} 7 & -1 \\ -1 & 3 \end{pmatrix}^{-1} \begin{pmatrix} 120 \\ 20 \end{pmatrix}$$

$$\therefore V_A = 19 \text{ V}, \quad V_B = 13 \text{ V}$$

$$= \begin{pmatrix} 19 \\ 13 \end{pmatrix}$$

$$V_x = V_A - V_B = 6 \text{ V}$$

$$P_{R4} = \frac{V^2}{R} = \frac{V_x^2}{R_4} = 3.6 \text{ mW}$$

5. (b)

By applying KCL to node A and B.

$$2 = \frac{V_A}{12.5} + \frac{V_A - V_B}{10} + \frac{V_A - 100}{200} \quad \text{--- (1)}$$

$$\frac{V_B - V_A}{10} + \frac{V_B}{50} + \frac{V_B - 100}{40} = 0 \quad \text{--- (2)}$$

After regrouping terms.

$$37V_A - 20V_B = 500 \quad \text{--- (1')}$$

$$-20V_A + 29V_B = 500 \quad \text{--- (2')}$$

So,

$$\begin{pmatrix} 37 & -20 \\ -20 & 29 \end{pmatrix} \begin{pmatrix} V_A \\ V_B \end{pmatrix} = \begin{pmatrix} 500 \\ 500 \end{pmatrix} \Rightarrow \begin{pmatrix} V_A \\ V_B \end{pmatrix} = \begin{pmatrix} 37 & -20 \\ -20 & 29 \end{pmatrix}^{-1} \begin{pmatrix} 500 \\ 500 \end{pmatrix}$$

$$\therefore V_A \approx 36.4(V) \quad V_B \approx 42.3(V)$$

And, the power delivered by voltage source is,

$$P_V = (-i_{S_2}) \cdot V_{S_2} = (-1.7) 100 = -170(W)$$

$\left(\because i_{S_2} = \frac{V_{S_2} - V_B}{R_2} + \frac{V_{S_2} - V_A}{R_1} \approx 1.7(A) \right)$

the Power delivered by current source is,

$$P_C = (-I_{S_2}) \cdot V_A = (-2) \cdot 36.4 = -72.8(W)$$

The Powers absorbed by each resistor are as follows.

$$P_{R_1} = \frac{(V_{S_2} - V_A)^2}{R_1} \approx 14.4(W), \quad P_{R_2} = \frac{(V_{S_2} - V_B)^2}{R_2} \approx 83.2(W)$$

$$P_{R_3} = \frac{V_B^2}{R_3} \approx 35.8(W) \quad P_{R_4} = \frac{V_X^2}{R_4} \approx 3.5(W) \quad P_{R_5} = \frac{V_A^2}{R_5} \approx 106(W)$$

$$\therefore \underbrace{(P_V + P_C)}_{\text{Power delivered}} + \underbrace{(P_{R_1} + P_{R_2} + P_{R_3} + P_{R_4} + P_{R_5})}_{\text{Power absorbed}} \approx 0$$