

HW 12 Solutions

P 8.2 [a] $-\alpha + \sqrt{\alpha^2 - \omega_o^2} = -250$

$$-\alpha - \sqrt{\alpha^2 - \omega_o^2} = -1000$$

Adding the above equations, $-2\alpha = -1250$

$$\alpha = 625 \text{ rad/s}$$

$$\frac{1}{2RC} = \frac{1}{2R(0.1 \times 10^{-6})} = 625$$

$$R = 8 \text{ k}\Omega$$

$$2\sqrt{\alpha^2 - \omega_o^2} = 750$$

$$4(\alpha^2 - \omega_o^2) = 562,500$$

$$\therefore \omega_o = 500 \text{ rad/s}$$

$$\omega_o^2 = 25 \times 10^4 = \frac{1}{LC}$$

$$\therefore L = \frac{1}{(25 \times 10^4)(0.1 \times 10^{-6})} = 40 \text{ H}$$

[b] $i_R = \frac{v(t)}{R} = -1e^{-250t} + 4e^{-1000t} \text{ mA}, \quad t \geq 0^+$

$$i_C = C \frac{dv(t)}{dt} = 0.2e^{-250t} - 3.2e^{-1000t} \text{ mA}, \quad t \geq 0^+$$

$$i_L = -(i_R + i_C) = 0.8e^{-250t} - 0.8e^{-1000t} \text{ mA}, \quad t \geq 0$$

P 8.3 [a] $i_R(0) = \frac{15}{200} = 75\text{mA}$

$$i_L(0) = -45\text{mA}$$

$$i_C(0) = -i_L(0) - i_R(0) = 45 - 75 = -30\text{mA}$$

[b] $\alpha = \frac{1}{2RC} = \frac{1}{2(200)(0.2 \times 10^{-6})} = 12,500$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(50 \times 10^{-3})(0.2 \times 10^{-6})} = 10^8$$

$$s_{1,2} = -12,500 \pm \sqrt{1.5625 \times 10^8 - 10^8} = -12,500 \pm 7500$$

$$s_1 = -5000\text{ rad/s}; \quad s_2 = -20,000\text{ rad/s}$$

$$v = A_1 e^{-5000t} + A_2 e^{-20,000t}$$

$$v(0) = A_1 + A_2 = 15$$

$$\frac{dv}{dt}(0) = -5000A_1 - 20,000A_2 = \frac{-30 \times 10^{-3}}{0.2 \times 10^{-6}} = -15 \times 10^4\text{V/s}$$

Solving, $A_1 = 10$; $A_2 = 5$

$$v = 10e^{-5000t} + 5e^{-20,000t}\text{ V}, \quad t \geq 0$$

[c] $i_C = C \frac{dv}{dt}$

$$= 0.2 \times 10^{-6}[-50,000e^{-5000t} - 100,000e^{-20,000t}]$$

$$= -10e^{-5000t} - 20e^{-20,000t}\text{ mA}$$

$$i_R = 50e^{-5000t} + 25e^{-20,000t}\text{ mA}$$

$$i_L = -i_C - i_R = -40e^{-5000t} - 5e^{-20,000t}\text{ mA}, \quad t \geq 0$$

P8.4 $\frac{1}{2RC} = \frac{1}{2(312.5)(0.2 \times 10^{-6})} = 8000$

$$\frac{1}{LC} = \frac{1}{(50 \times 10^{-3})(0.2 \times 10^{-6})} = 10^8$$

$$s_{1,2} = -8000 \pm \sqrt{8000^2 - 10^8} = -8000 \pm j6000 \text{ rad/s}$$

\therefore response is underdamped

$$v(t) = B_1 e^{-8000t} \cos 6000t + B_2 e^{-8000t} \sin 6000t$$

$$v(0^+) = 15 \text{ V} = B_1; \quad i_R(0^+) = \frac{15}{312.5} = 48 \text{ mA}$$

$$i_C(0^+) = [-i_L(0^+) + i_R(0^+)] = -[-45 + 48] = -3 \text{ mA}$$

$$\frac{dv(0^+)}{dt} = \frac{-3 \times 10^{-3}}{0.2 \times 10^{-6}} = -15,000 \text{ V/s}$$

$$\frac{dv(0)}{dt} = -8000B_1 + 6000B_2 = -15,000$$

$$6000B_2 = 8000(15) - 15,000; \quad \therefore B_2 = 17.5 \text{ V}$$

$$v(t) = 15e^{-8000t} \cos 6000t + 17.5e^{-8000t} \sin 6000t \text{ V}, \quad t \geq 0$$

7 [a] $\alpha = 20,000$; $\omega_d = 15,000$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2}$$

$$\therefore \omega_o^2 = \omega_d^2 + \alpha^2 = 225 \times 10^6 + 400 \times 10^6 = 625 \times 10^6$$

$$\frac{1}{LC} = 625 \times 10^6$$

$$L = \frac{1}{(625 \times 10^6)(40 \times 10^{-9})} = 40 \text{ mH}$$

[b] $\alpha = \frac{1}{2RC}$

$$\therefore R = \frac{1}{2\alpha C} = \frac{1}{2(20,000)(40 \times 10^{-9})} = 625 \Omega$$

[c] $V_o = v(0) = 100 \text{ V}$

[d] $I_o = i_L(0) = -i_R(0) - i_C(0)$

$$i_R(0) = \frac{V_o}{R} = \frac{100}{625} = 160 \text{ mA}$$

$$i_C(0) = C \frac{dv}{dt}(0)$$

$$\frac{dv}{dt} = 100 \{ e^{-20,000t} [-15,000 \sin 15,000t - 30,000 \cos 15,000t] -$$

$$20,000 e^{-20,000t} [\cos 15,000t - 2 \sin 15,000t]$$

$$\frac{dv}{dt}(0) = 100 \{ 1(-30,000) - 20,000 \} = -500 \times 10^4$$

$$C \frac{dv}{dt}(0) = -500 \times 10^4 (40 \times 10^{-9}) = -200 \text{ mA}$$

$$\therefore I_o = 200 - 160 = 40 \text{ mA}$$

[e] $\frac{dv}{dt} = 100 e^{-20,000t} [25,000 \sin 15,000t - 50,000 \cos 15,000t]$

$$= 25 \times 10^5 e^{-20,000t} [\sin 15,000t - 2 \cos 15,000t]$$

$$C \frac{dv}{dt} = 0.1 e^{-20,000t} (\sin 15,000t - 2 \cos 15,000t)$$

$$i_C(t) = 0.1 e^{-20,000t} (\sin 15,000t - 2 \cos 15,000t) \text{ A}$$

$$i_R(t) = 0.16 e^{-20,000t} (\cos 15,000t - 2 \sin 15,000t) \text{ A}$$

$$i_L(t) = -i_R(t) - i_C(t)$$

$$= e^{-20,000t} (40 \cos 15,000t + 220 \sin 15,000t) \text{ mA}, \quad t \geq 0$$