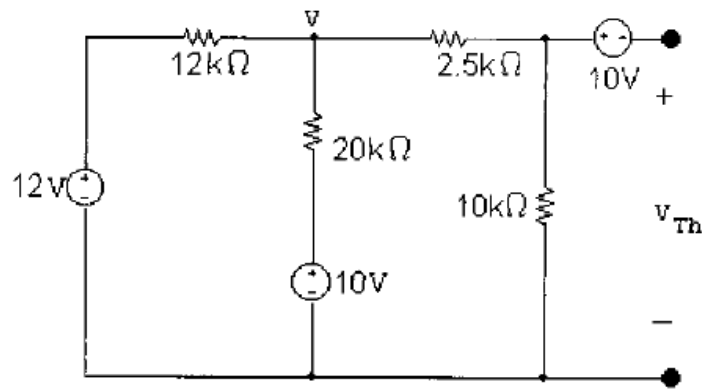


## HW#8 Solutions

P4.77 [a]




$$\frac{v - 12}{12,000} + \frac{v - 10}{20,000} + \frac{v}{12,500} = 0$$

Solving,  $v = 7.03125 \text{ V}$

$$v_{10k} = \frac{10,000}{12,500} (7.03125) = 5.625 \text{ V}$$

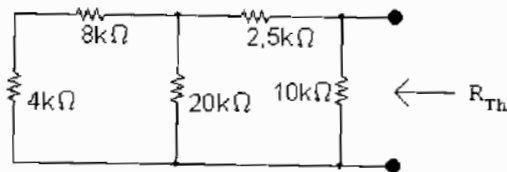
$$\therefore V_{Th} = v - 10 = -4.375 \text{ V}$$



$$R_{Th} = [(12,000 || 20,000) + 2500] = 5 \text{ k}\Omega$$


$$R_o = R_{Th} = 5 \text{ k}\Omega$$

[b]

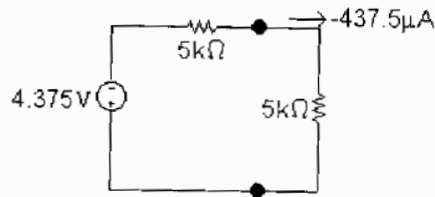

$$p_{max} = (-437.5 \times 10^{-6})^2 (5000) = 957.03 \mu \text{ W}$$

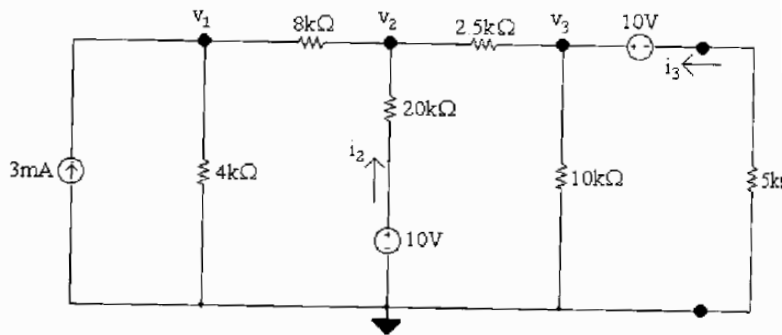P 4.78 Write KCL equations at each of the labeled nodes, place them in standard form, and solve:



$$\text{At } v_1: \quad -3 \times 10^{-3} + \frac{v_1}{4000} + \frac{v_1 - v_2}{8000} = 0$$

$$\text{At } v_2: \quad \frac{v_2 - v_1}{8000} + \frac{v_2 - 10}{20,000} + \frac{v_2 - v_3}{2500} = 0$$

$$\text{At } v_3: \quad \frac{v_3 - v_2}{2500} + \frac{v_3}{10,000} + \frac{v_3 - 10}{5000} = 0$$

Standard form:

$$v_1 \left( \frac{1}{4000} + \frac{1}{8000} \right) + v_2 \left( -\frac{1}{8000} \right) + v_3(0) = 0.003$$

$$v_1 \left( -\frac{1}{8000} \right) + v_2 \left( \frac{1}{8000} + \frac{1}{20,000} + \frac{1}{2500} \right) + v_3 \left( -\frac{1}{2500} \right) = \frac{10}{20,000}$$

$$v_1(0) + v_2 \left( -\frac{1}{2500} \right) + v_3 \left( \frac{1}{2500} + \frac{1}{10,000} + \frac{1}{5000} \right) = \frac{10}{5000}$$

Calculator solution:

$$v_1 = 10.890625 \text{ V} \quad v_2 = 8.671875 \text{ V} \quad v_3 = 7.8125 \text{ V}$$

Calculate currents:

$$i_2 = \frac{10 - v_2}{20,000} = 66.40625 \mu\text{A} \quad i_3 = \frac{10 - v_3}{5000} = 437.5 \mu\text{A}$$

Calculate power delivered by the sources:

$$p_{3\text{mA}} = (3 \times 10^{-3})v_1 = (3 \times 10^{-3})(10.890625) = 32.671875 \text{ mW}$$

$$p_{10\text{Vmiddle}} = i_2(10) = (66.40625 \times 10^{-6})(10) = 0.6640625 \text{ mW}$$

$$p_{10\text{Vtop}} = i_3(10) = (437.5 \times 10^{-6})(10) = 4.375 \text{ mW}$$

$$p_{\text{deliveredtotal}} = 32.671875 + 0.6640625 + 4.375 = 37.7109375 \text{ mW}$$

Calculate power absorbed by the 5 kΩ resistor and the percentage power:


$$p_{5\text{k}} = i_3^2(5000) = (437.5 \times 10^{-6})^2(5000) = 0.95703125 \text{ mW}$$

$$\% \text{ delivered to } R_o: \quad \frac{0.95793125}{37.7109375}(100) = 2.54\%$$

86 [a] Since  $0 \leq R_o < \infty$  maximum power will be delivered to the  $8 \Omega$  resistor when  $R_o = 0$ .

[b]  $P = \frac{24^2}{8} = 72 \text{ W}$

P 4.90 Voltage source acting alone:

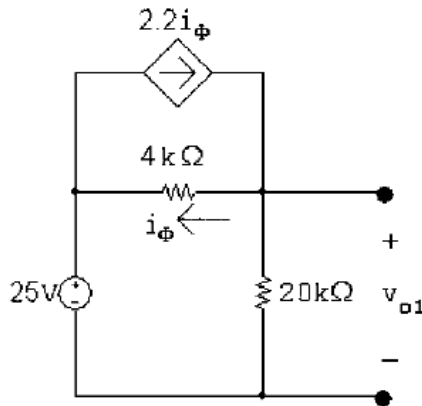


$$\frac{v_{o1} - 25}{4000} + \frac{v_{o1}}{20,000} - 2.2 \left( \frac{v_{o1} - 25}{4000} \right) = 0$$

Simplifying  $5v_{o1} - 125 + v_{o1} - 11v_{o1} + 275 = 0$

$\therefore v_{o1} = 30 \text{ V}$

Current source acting alone:

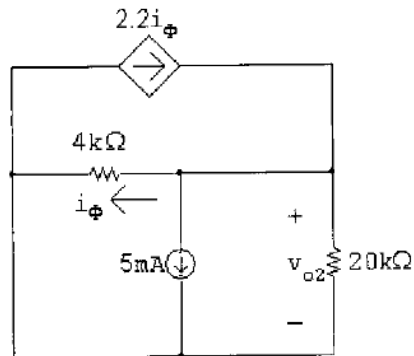


$$\frac{v_{o2}}{4000} + \frac{v_{o2}}{20,000} + 0.005 - 2.2 \left( \frac{v_{o2}}{4000} \right) = 0$$

Simplifying  $5v_{o2} + v_{o2} + 100 - 11v_{o2} = 0$

$\therefore v_{o2} = 20 \text{ V}$

$v_o = v_{o1} + v_{o2} = 30 + 20 = 50 \text{ V}$


P 4.91 Voltage source acting alone:

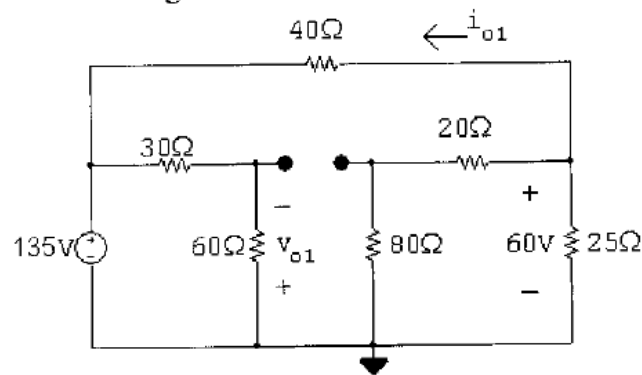

$$i_{o1} = \frac{-135}{40 + 100 \parallel 25} = -2.25 \text{ A}$$

$$v_{o1} = \frac{60}{90}(-135) = -90 \text{ V}$$

Current source acting alone:

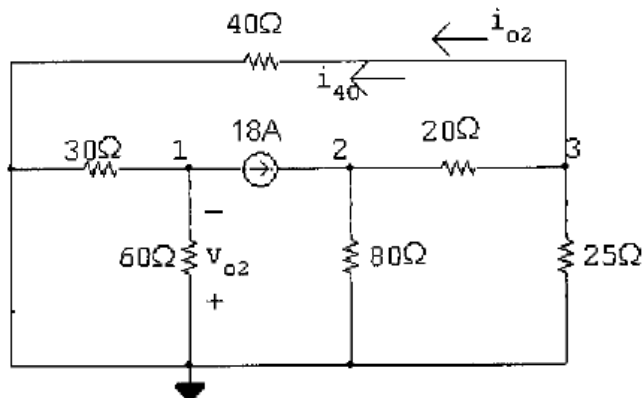

$$\frac{v_1}{30} + \frac{v_1}{60} + 18 = 0 \quad \therefore \quad v_1 = -360 \text{ V}; \quad v_{o2} = 360 \text{ V}$$

$$-18 + \frac{v_2}{80} + \frac{v_2 - v_3}{20} = 0$$

$$\frac{v_3 - v_2}{20} + \frac{v_3}{25} + \frac{v_3}{40} = 0$$

$$\therefore \quad v_2 = 441.6 \text{ V}; \quad v_3 = 192 \text{ V}; \quad i_{o2} = 192/40 = 4.8 \text{ A}$$

$$\therefore \quad v_o = v_{o1} + v_{o2} = -90 + 360 = 270 \text{ V}$$

$$i_o = i_{o1} + i_{o2} = -2.25 + 4.8 = 2.55 \text{ A}$$